 




Introducción a VLSI

EAMTA 2006






Introducción a VLSI

Clase 3: Lógica Combinacional y Secuencial

Programa

 - El Transistor MOS
- Layers y Layout
- **Lógica Combinacional**
- Lógica Secuencial y Subsistemas




Organización


- Tiempos de propagación y retardo
- Lógica Combinacional
- Lógica “ratioed”
- Lógica dinámica
- Lógica estática
- Propiedades de compuertas CMOS
- Lógica secuencial

Propagation delay

Delay definitions

 


 - Delay time (t_d or t_{pd}) -- Delay between when the input signal to a gate reaches the 50% point and when the output signal reaches the 50% point.
- Rise time (t_r) -- time it takes for a signal to go from 10% to 90% of its output range
- Fall time (t_f) -- time it takes for a signal to go from 90% to 10% of its output range




Delay cause

 - Gate delays are determined by how quickly the driving gate can charge/discharge its load capacitance




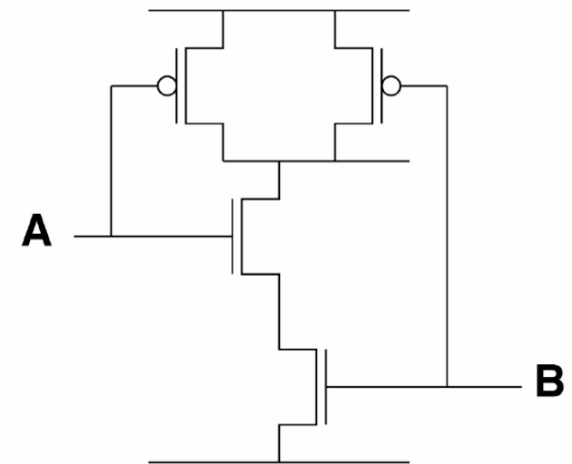- Gate delay may vary depending on which inputs are changing -- generally use the worst case





How to handle a big circuit

 - Divide circuit into *DC-connected components*, solve for each component



Fall time analysis

  During the fall time one or more nMOS transistors discharge the energy stored in the output capacitance





x_1 : Initial Operating Point

x_3 : Operating Point after Completion of Switching

Fall time analysis

  
During the fall time, the nMOS transistor starts in the saturated region and passes into the linear region



Fall time analysis

Divide fall time into two components: $t_{f,sat}$ and $t_{f,linear}$

 In saturation, current through the transistor is constant



$$C_L \frac{dV_o}{dt} = -I_{dsn} = -\frac{\beta_n}{2}(V_{dd} - V_{tn})^2$$

This becomes

$$\frac{-2C_L}{\beta_n(V_{dd} - V_{tn})^2} dV_o = dt$$

Define t_1 , t_2 such that $V_o(t_1) = 0.9V_{dd}$ and $V_o(t_2) = V_{dd} - V_t$. Then,

$$\frac{-2C_L}{\beta_n(V_{dd} - V_{tn})^2} \int_{0.9V_{dd}}^{V_{dd}-V_{tn}} dV_o = \int_{t_1}^{t_2} dt = t_2 - t_1$$

And $t_{f,sat}$ is:

$$\frac{2C_L(V_{tn} - 0.1V_{dd})}{\beta_n(V_{dd} - V_{tn})^2}$$

Fall time analysis

In the linear region, current through the transistor depends on V_o

$$C_L \frac{dV_o}{dt} = -I_{dsn} = -\beta_n \left[(V_{dd} - V_{tn})V_o - \frac{1}{2}V_o^2 \right]$$

And $t_{f, \text{linear}}$ becomes

$$\frac{C_L}{\beta_n(V_{dd} - V_{tn})} \int_{0.1V_{dd}}^{V_{dd}-V_{tn}} \frac{dV_o}{\frac{V_o^2}{2(V_{dd}-V_{tn})} - V_o}$$

Integrating, we get $t_{f, \text{linear}} = \frac{C_L}{\beta_n(V_{dd} - V_{tn})} \ln \left(\frac{19V_{dd} - 20V_{tn}}{V_{dd}} \right)$
And

$$t_f = \frac{2C_L}{\beta_n(V_{dd} - V_{tn})} \times \left[\frac{V_{tn} - 0.1V_{dd}}{V_{dd} - V_{tn}} + \frac{1}{2} \ln \left(\frac{19V_{dd} - 20V_{tn}}{V_{dd}} \right) \right]$$

For many processes, $V_t \approx 0.2V_{dd}$, allowing us to approximate

$$t_f \approx \frac{4C_L}{\beta_n V_{dd}}$$

Rise time analysis

Redoing the same analysis for the pMOS transistor in pull-up gives

$$t_r \approx \frac{4C_L}{\beta_p V_{dd}}$$

Note that beta for pMOS tends to be about 1/2 beta for nMOS given equivalent size devices, so typically want pMOS about twice as wide as nMOS to get equivalent rise and fall times

Gate delay estimation

Somewhat more complicated -- depends on rise and fall times of the input signals.

Assuming (unrealistically) that the input rises or falls in zero time, then the gate delay can be approximated as half of the rise or fall time for the gate, and averaged to

$$t_d \approx \frac{t_r + t_f}{4}$$

Since gates are generally driven by other gates, we need a better approximation for real circuits

Could just simulate the design, but that wouldn't give much insight

- Simulation is good for verifying that something works the way you want but not for designing it to do so

Circuit delay estimation

1. Divide circuit into DC-connected blocks as we talked about at the start of lecture.
2. Compute a simple delay model for each block
3. Add the delays for each block to get overall delay.

In CMOS, a DC-connected block (stage) will be either:

1. A single logic gate
2. A transmission-gate network and the gates driving it

In the simple case, a block switches in response to a single signal changing at one of its inputs, called the *trigger* signal

Simplifying the problem

As we've seen, solving even simple transistor networks analytically requires solving differential equations that change at region boundaries

- For example, the rise and fall time derivations we presented really only apply for inverters, and computing them for larger gates is more complex
- Now think about doing that for a 100-transistor network, much less anything bigger

Solution: *linearize* the transistor equations by replacing each transistor with an equivalent resistor, R_{eff}

Computing R_{eff}

R_{eff} for a transistor depends on what region it's operating in

- Example: $R_{eff} = dV_{ds}/dI_{ds} = \text{infinity}$ in saturation
- In linear region, $\frac{1}{R_{eff}} \triangleq \left. \frac{dI_{ds}}{dV_{ds}} \right|_{V_{ds}=0} \approx \beta(V_{gs} - V_t)$


During switching, a transistor travels through different regions of operation

We want a single R_{eff} that approximates the behavior of a transistor during the entire rise/fall time

- R_{eff} will be different depending on whether the transistor is transmitting a zero or a one.


NMOS transistor, logic 0

 nMOS transistor, discharging capacitor to ground



NMOS transistor, logic 0

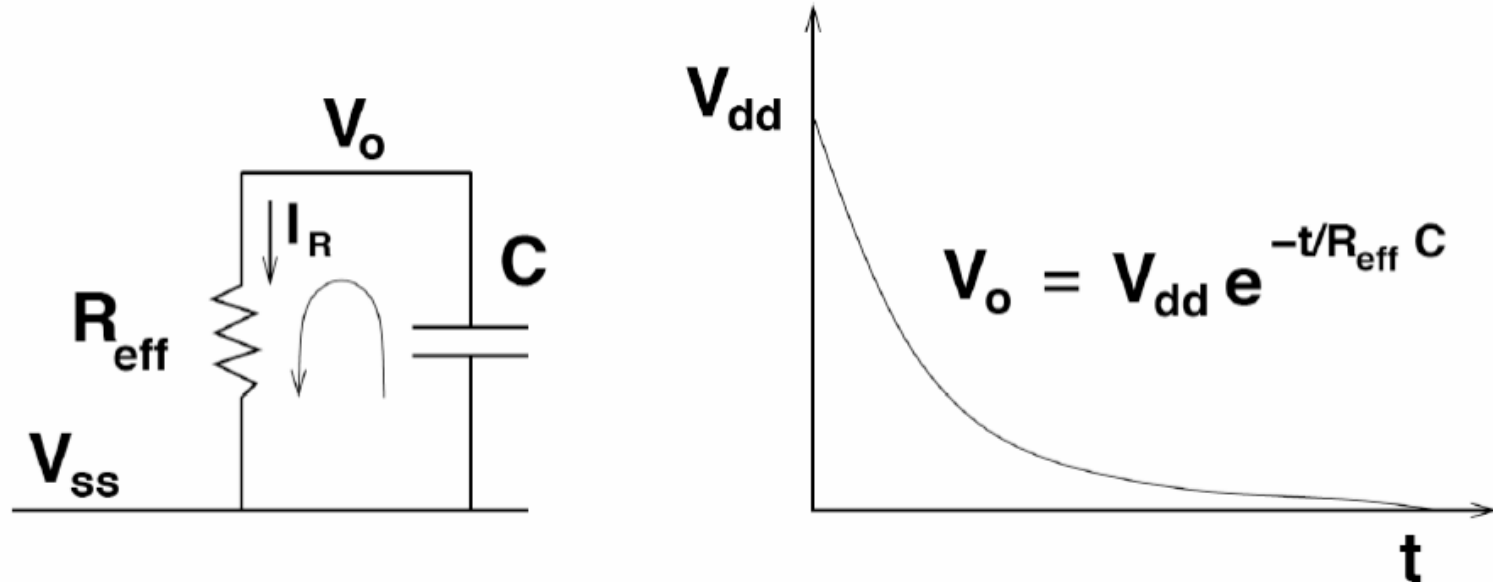- Want to model as a single network with R_{eff} , C





- Choose R_{eff} so that both circuits have the same fall time

$$\frac{4}{\beta_n V_{dd}} C \approx t_f = \ln(9) R_{\text{eff}} C \Rightarrow R_{\text{eff}} = \frac{4 / \ln(9)}{\beta_n V_{dd}} \approx \frac{1.82}{\beta_n V_{dd}}$$

NMOS transistor, logic 1

Back to the I-V curve

 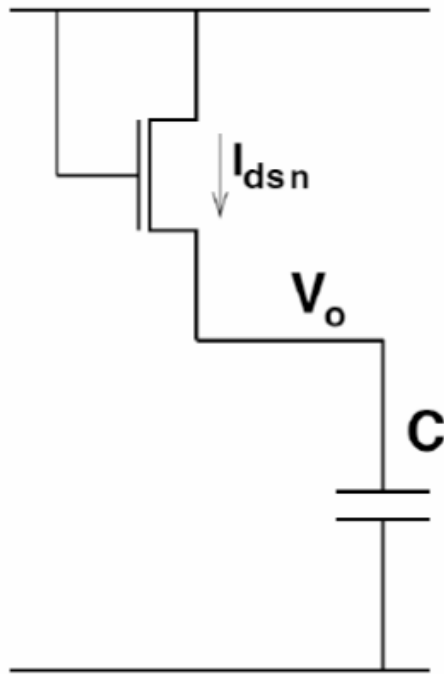

NMOS transistor, logic 1

Problem: V_O never makes it to $0.9 V_{dd}$ in this case, assuming $V_t = 0.2V_{dd}$, so can't try to match the full rise time

If we try to match the time it takes to hit $0.5V_{dd}$, we get

$$R_{eff} \approx \frac{25/[6 \ln(2)]}{\beta_n V_{dd}} \approx \frac{6.0}{\beta_n V_{dd}}$$

Note that this is about 3x larger than the discharging case. Why does this make sense?

PMOS transistors

Similar expressions can be derived for a pMOS transistor, using β_p instead of β_n .


pMOS transmitting a logic 1:

$$R_{eff} = \frac{4/\ln(9)}{\beta_p V_{dd}} \approx \frac{1.82}{\beta_p V_{dd}}$$

pMOS transmitting a logic 0:

$$R_{eff} \approx \frac{25/[6\ln(2)]}{\beta_p V_{dd}} \approx \frac{6.0}{\beta_p V_{dd}}$$


Example of the process

 

Estimating stage delay

Need to decide whether each transistor is off, transmitting a logic 0, or transmitting a logic 1.

 Then, can replace the stage with an RC network



using Elmore Delay formula

$$\tau_1 = R_1 C_1$$

$$\tau_2 = R_1 C_2$$

$$\tau_3 = (R_1 + R_3) C_3$$

$$\tau_4 = R_1 C_4$$

$$\tau_5 = (R_1 + R_3 + R_5) C_5$$

$$\tau_6 = (R_1 + R_3) C_6$$

$$\tau_{eq} = \tau_1 + \tau_2 + \tau_3 + \tau_4 + \tau_5 + \tau_6$$

This is *still* too complex -- solving these networks exactly requires solving several simultaneous differential equations.


Simplify further by reducing to an equivalent single-RC network with time constant $\tau_{eq} = R_{eq} C_{eq}$

Elmore delay method

1. Identify an input node and an output node, and the unique path between them. Call the path P
2. For every node n in the tree other than the input node
 1. Identify the unique path between the input node and n
 2. Identify the sub-path that is the intersection of this path and P
 3. Sum the resistances along the sub-path, call it R_n
 4. If C_n is the capacitance at n , create a $\tau_n = R_n C_n$
3. Sum the τ_n to get τ_{eq} for the network
4. Given τ_{eq} , can select R_{eq} and C_{eq} values to match, but generally don't need to, τ_{eq} is enough

Cascades

Suppose stage 1 feeds stage 2

 

If the time constant of stage 1 is τ_1 , when is stage 2 *triggered*? (I.e., when does it start switching)

Time for yet another approximation

Cascades

By convention, assume that stage 2 is triggered when the output of stage 1 has completed 90% of its logic swing and is thus well within V_t of one of the rails

Thus, the delay through stage 1 is

$$\tau_{d1} = \ln(10)\tau_{eq1} \approx 2.3\tau_{eq1}$$

Thus, if stage 1 triggers at time 0, stage 2 triggers at time $2.3 \tau_1$, stage 3 triggers at time $2.3 \tau_1 + 2.3 \tau_2$, etc.

Device sizing: the inverter

Device Sizing

- Assuming a symmetrical inverter, the capacitance is composed of:

$$C_L = C_{\text{int}} + C_{\text{ext}}$$

- C_{int} is the self-load, associated with diffusion and gate-drain (Miller)
- C_{ext} is extrinsic, load, wiring, etc.

$$t_p = 0.69 R_{eq} (C_{\text{int}} + C_{\text{ext}}) = t_{p0} (1 + C_{\text{ext}} / C_{\text{int}})$$

- where $t_{p0} = 0.69 R_{eq} C_{\text{int}}$ is the intrinsic delay ($C_{\text{ext}}=0$)

- What are the consequences of scaling ?

Device Sizing


- C_{int} scales with size ratio S , and also R_{eq} :

$$C_{int} = SC_{iref}, \quad R_{eq} = R_{iref} / S,$$

- The delay is: $t_p = t_{p0}(1 + C_{ext} / SC_{iref})$


- **Intrinsic delay is independent of sizing** and is determined by technology and layout.
- S infinitely large gives eliminates the impact of an external load
 - (Yet, a big enough sizing produces similar results with less Silicon area)
- A big inverter has **big input capacitance** and affects the previous stages !

Device Sizing

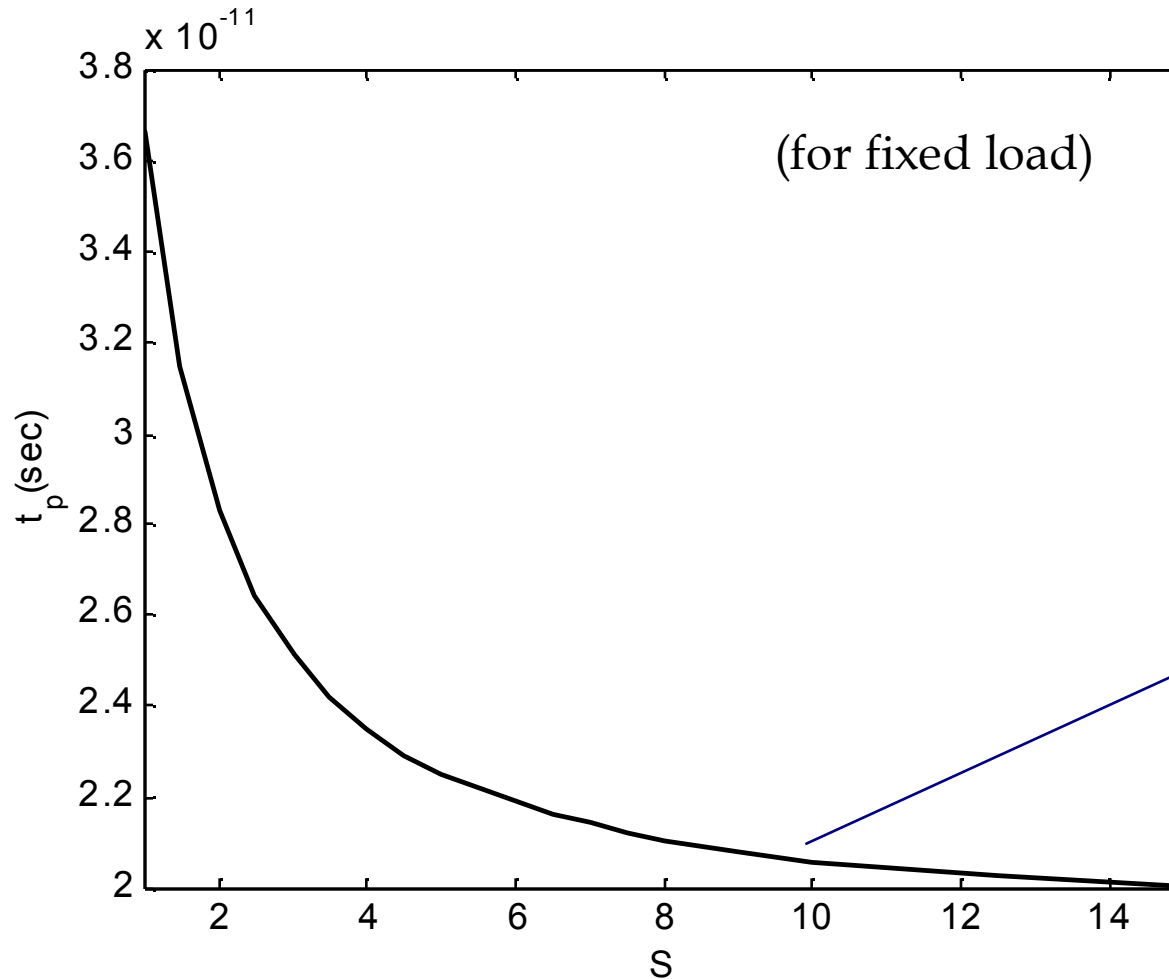

Self-loading effect:
Intrinsic capacitances
dominate

Inverter chain sizing

 

If C_L is given:

- How many stages are needed to minimize the delay?
- How to size the inverters?

May need some additional constraints.

$$\text{Delay} \sim R_W (C_{int} + C_L)$$


$$t_p = kR_W C_{int} (1 + C_L / C_{int}) = t_{p0} (1 + f / \gamma)$$

$$C_{int} = \gamma C_{gin} \text{ with } \gamma \approx 1$$

$$f = C_L / C_{gin} - \text{effective fanout}$$

Delay is only a function of the ratio between its external load capacitance and its input capacitance

Apply to Inverter Chain

 

$$t_p = t_{p1} + t_{p2} + \dots + t_{pN}$$

$$t_{pj} \sim R_{unit} C_{unit} \left(1 + \frac{C_{gin,j+1}}{\gamma C_{gin,j}} \right)$$


$$t_p = \sum_{j=1}^N t_{p,j} = t_{p0} \sum_{i=1}^N \left(1 + \frac{C_{gin,j+1}}{\gamma C_{gin,j}} \right), \quad C_{gin,N+1} = C_L$$

Optimum: When each stage is sized by f and has same eff. fanout f :

$$f^N = F = C_L / C_{gin,1}$$

$$f = \sqrt[N]{F}$$





Example

 

C_L/C_1 has to be evenly distributed across $N = 3$ stages:


$$f = \sqrt[3]{8} = 2$$

Buffer Design

    	N	f	t_p
	1	64	65
	2	8	18
	3	4	15
	4	2.8	15.3


Lógica Combinacional

Combinational vs. Sequential Logic

 

Combinational

$$\text{Output} = f(\text{In})$$

 

Sequential

$$\text{Output} = f(\text{In}, \text{Previous In})$$


Static CMOS Circuit

At every point in time (except during the switching transients) each gate output is connected to either V_{DD} or V_{ss} via a low-resistive path.

The outputs of the gates assume at all times the value of the Boolean function, implemented by the circuit (ignoring, once again, the transient effects during switching periods).

This is in contrast to the *dynamic* circuit class, which relies on temporary storage of signal values on the capacitance of high impedance circuit nodes.

Static Complementary CMOS

 


PUN and PDN are **dual** logic networks

NMOS Transistors in Series/Parallel Connection

Transistors can be thought as a switch controlled by its gate signal


 
NMOS switch closes when switch control input is high



NMOS Transistors pass a “strong” 0 but a “weak” 1

PMOS Transistors in Series/Parallel Connection

 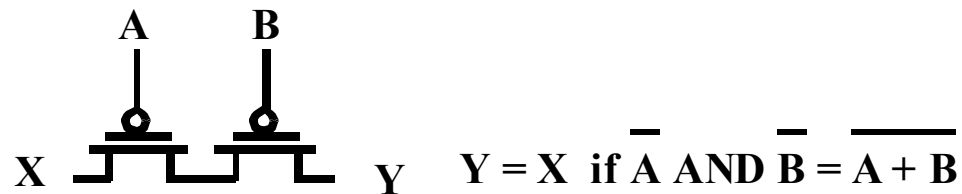PMOS switch closes when switch control input is low



PMOS Transistors pass a “strong” 1 but a “weak” 0


Complementary CMOS Logic Style

- PUP is the DUAL of PDN
(can be shown using DeMorgan's Theorem's)

$$\overline{A + B} = \bar{A}\bar{B}$$

$$\overline{AB} = \bar{A} + \bar{B}$$

- The complementary gate is inverting

 


AND = NAND + INV

Example Gate: NAND

A	B	Out
0	0	1
0	1	1
1	0	1
1	1	0

Truth Table of a 2 input NAND gate

 

PDN: $G = A B \Rightarrow$ Conduction to GND


PUN: $F = \overline{A} + \overline{B} = \overline{AB} \Rightarrow$ Conduction to V_{DD}

$$\overline{G(In_1, In_2, In_3, \dots)} \equiv F(\overline{In_1}, \overline{In_2}, \overline{In_3}, \dots)$$


Example Gate: NOR

A	B	Out
0	0	1
0	1	0
1	0	0
1	1	0


Truth Table of a 2 input NOR gate

 


Complex CMOS Gate

 


Constructing a Complex Gate

 

(a) pull-down network

 

 (b) Deriving the pull-up network hierarchically by identifying sub-nets



(c) complete gate

Cell Design


■ Standard Cells

- ☐ General purpose logic
- ☐ Can be synthesized
- ☐ Same height, varying width

■ Datapath Cells

- ☐ For regular, structured designs (arithmetic)
- ☐ Includes some wiring in the cell
- ☐ Fixed height and width

Standard cells

 


Cell height 12 metal tracks
 Metal track is approx. $3\lambda + 3\lambda$
 Pitch =
 repetitive distance between objects

Cell height is "12 pitch"



Rails $\sim 10\lambda$

Standard cells

?

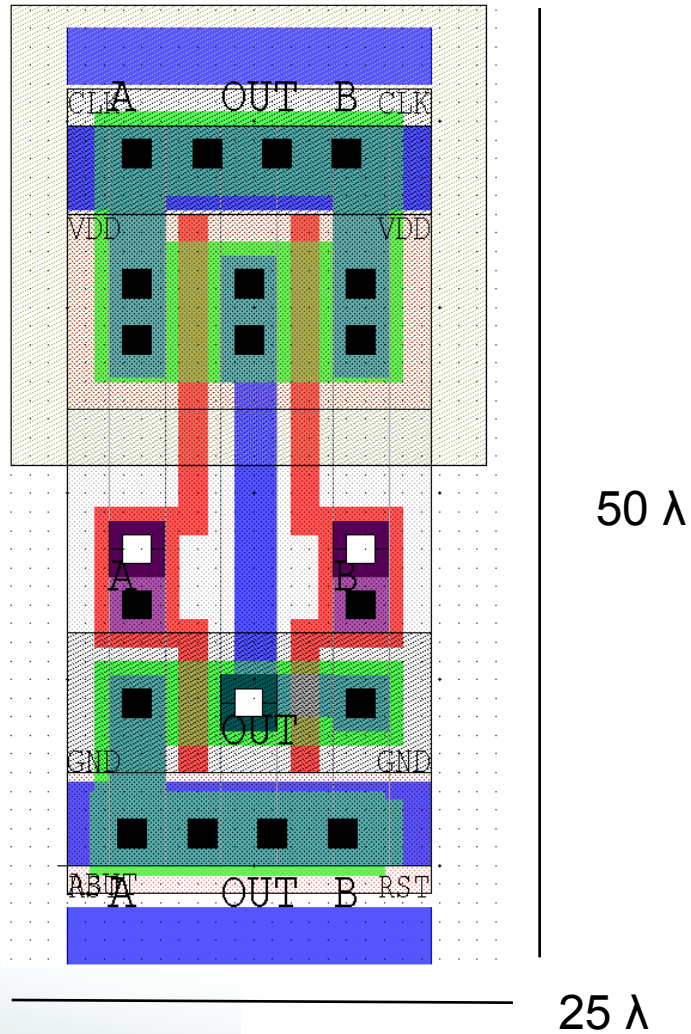

Standard cells

  

?



50 λ

30 λ


Stick Diagrams

Contains no dimensions

  
Represents relative positions of transistors




Stick Diagrams

 



$$X = C \cdot (A + B)$$

 

Logic Graph

 

Two Versions of $C \cdot (A + B)$

  


Permutation of input signals that produce uninterrupted active strips is important !



Euler Paths

- There is a systematic approach to uninterrupted strips of active.
Two steps:
- Step 1: Construction of logic graph
- Step 2: Identification of Euler graphs
- Euler path is a path through all nodes such that every edge is visited once.
- Euler path is equivalent to an uninterrupted A-strip (successive S and D connections)
- Consistency: Same ordering for PUN and PDN


Euler Path

 


OAI22 Logic Graph

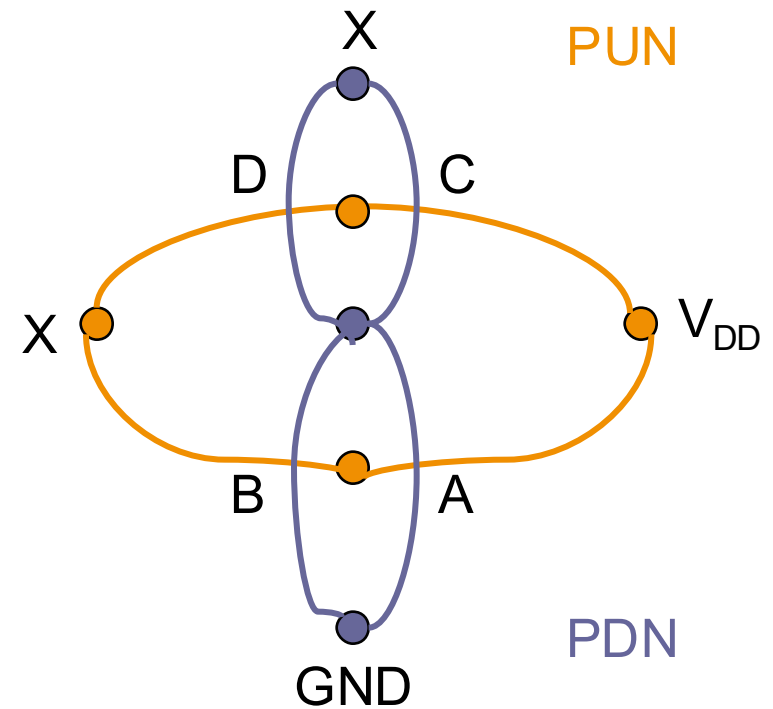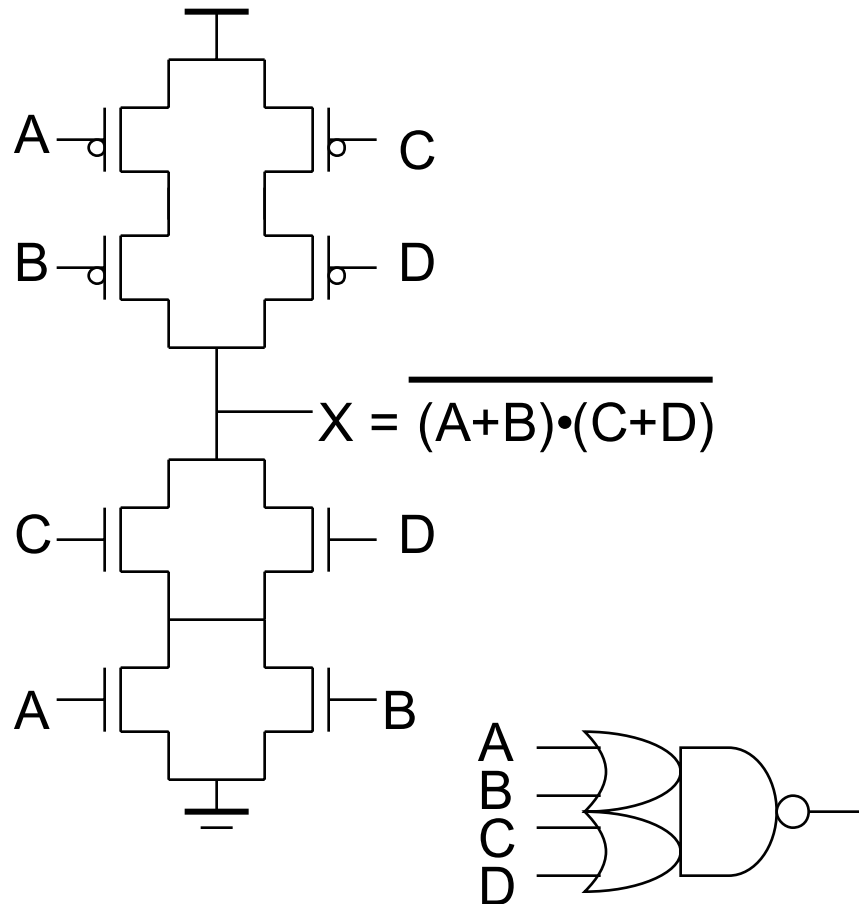


Example: $x = ab + cd$

 

 (a) Logic graphs for $\overline{(ab+cd)}$



(b) Euler Paths $\{a b c d\}$


 


(c) stick diagram for ordering $\{a b c d\}$

Properties of CMOS gates





Static Properties

- Depend on input pattern

 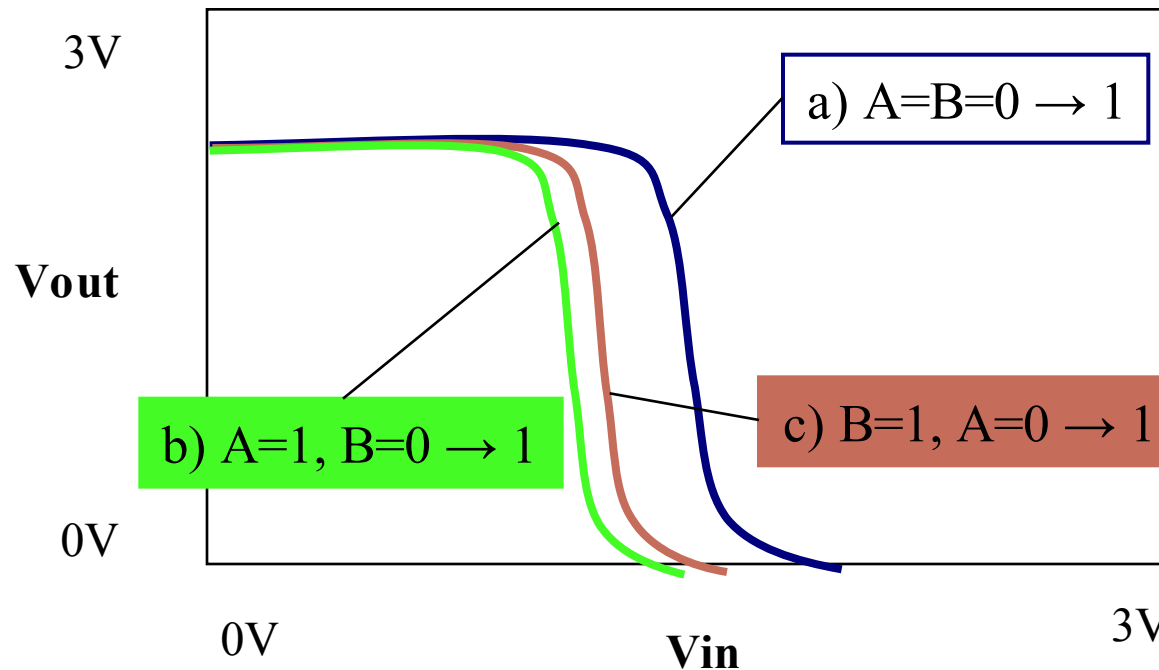


- a) Two pull-up transistors in parallel are more difficult to turn off than one
- b) One pull-up transistor, one pull-down. Dynamically, the internal node has to be discharge (slower)
- c) V_{ds1} produces bulk effect during discharge. More V_{in} is needed

Switch Delay Model

  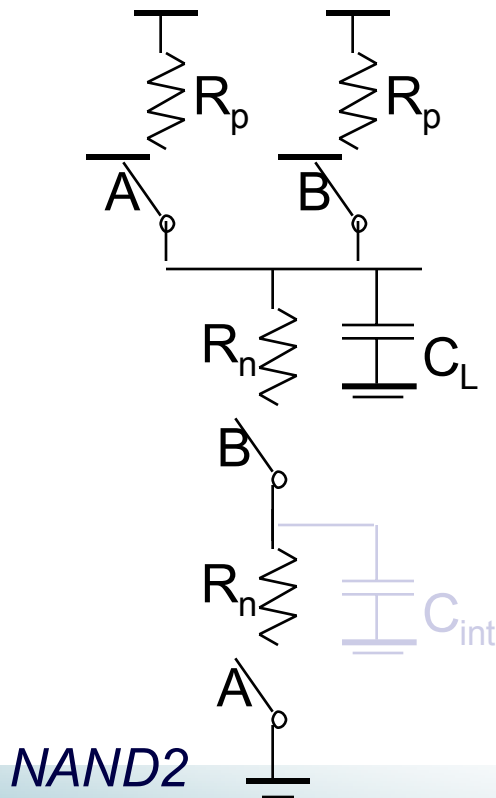
 


Input Pattern Effects on Delay

 


- Delay is dependent on the **pattern** of inputs
- Low to high transition
 - both inputs go low
 - delay is $0.69 R_p / 2 C_L$
 - one input goes low
 - delay is $0.69 R_p C_L$
 - when N transistor A goes off, internal node has to be charged
- High to low transition
 - both inputs go high
 - delay is $0.69 2R_n C_L$

Transistor Sizing

 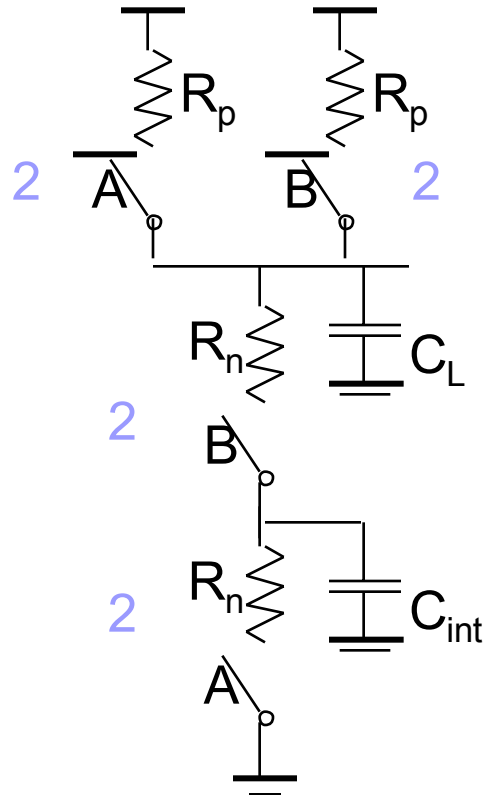


NAND based implementations are preferred over NOR ...

Transistor Sizing a Complex CMOS Gate

 

$$\text{OUT} = \overline{D + A \cdot (B + C)}$$

Fan-In Considerations

 


Distributed RC model
(Elmore delay)

$$t_{pHL} = 0.69 R_e (C_1 + 2C_2 + 3C_3 + 4C_L) \\ = R_e C_1 + 2 R_e C_2 + 3R_e C_3 + 4R_e C_L$$

* Propagation delay deteriorates rapidly as a function of fan-in – **quadratically** in the worst case. (prop. to $R \times C$)

* Internal nodes important !!

t_p as a Function of Fan-In

 


Intrinsic C increases linearly

Series transistors cause a double slowdown

Parallel transistors increase C

Gates with a fan-in greater than 4 should be avoided.

t_p as a Function of Fan-Out

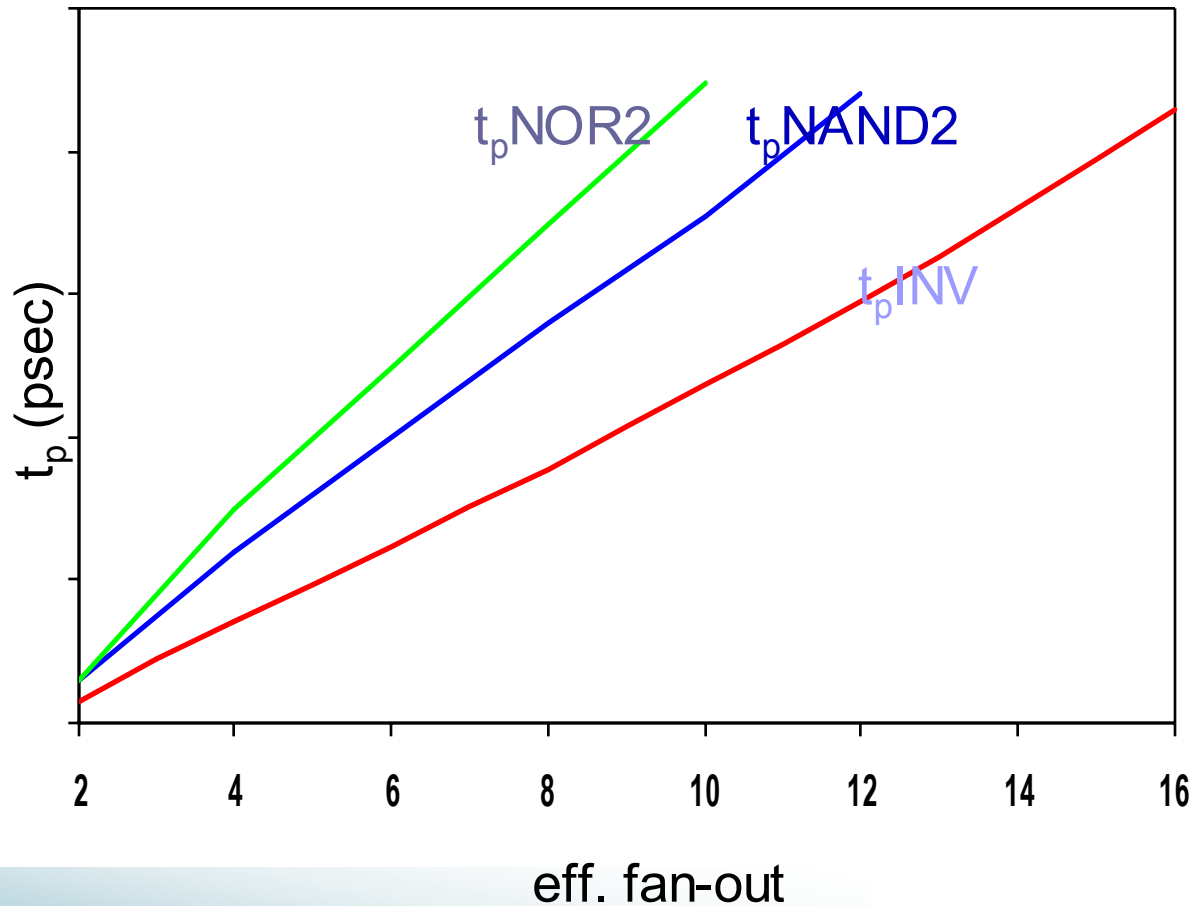

All gates have the same drive current.

Slope is a function of “driving strength”


t_p as a Function of Fan-In and Fan-Out

- Fan-in: **quadratic** due to increasing resistance and capacitance
- Fan-out: each additional fan-out gate adds **two** gate capacitances to C_L


$$t_p = a_1 FI + a_2 FI^2 + a_3 FO$$

Ratioed Logic


Ratioed Logic

 

(a) resistive load

 


(b) depletion load NMOS

 

(c) pseudo-NMOS

Goal: to reduce the number of devices over complementary CMOS


Ratioed Logic

 

- **N transistors + Load**
- $V_{OH} = V_{DD}$
- $V_{OL} = \frac{R_{PN}}{R_{PN} + R_L}$
- **Assymetrical response**
- **Static power consumption**
- $t_{pL} = 0.69 R_L C_L$


Active Loads

Depletion Load

 


depletion load NMOS

PMOS Load

 

pseudo-NMOS

Pseudo-NMOS

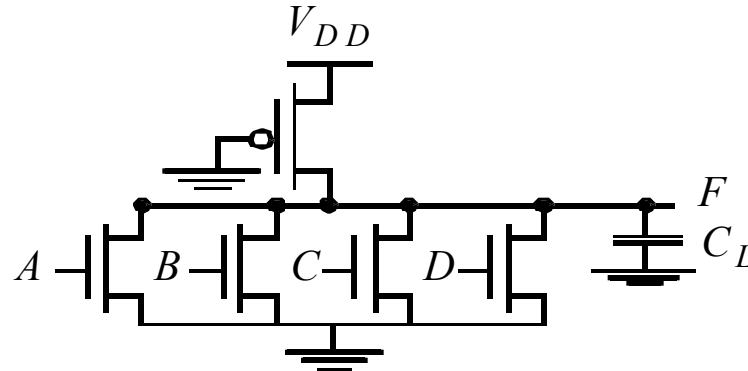


$$V_{OH} = V_{DD} \text{ (similar to complementary CMOS)}$$

$$k_n \left((V_{DD} - V_{Tn})V_{OL} - \frac{V_{OL}^2}{2} \right) = \frac{k_p}{2} (V_{DD} - |V_{Tp}|)^2$$

$$V_{OL} = (V_{DD} - V_T) \left[1 - \sqrt{1 - \frac{k_p}{k_n}} \right] \text{ (assuming that } V_T = V_{Tn} = |V_{Tp}|)$$

SMALLER AREA & LOAD BUT STATIC POWER DISSIPATION!!!

Pseudo-NMOS VTC

 


The bigger P , the faster the L to H transition, but more power and higher V_{ol}

Performance of a P-NMOS inverter

Size	Vol	Static P	Tplh
4	0.693	564 μ W	14 ps
2	0.273	298 μ W	56 ps
1	0.133	160 μ W	123 ps
$\frac{1}{2}$	0.064	80 μ W	268 ps
$\frac{1}{4}$	0.031	41 μ W	569 ps


Pass-Transistor Logic

Pass-Transistor Logic


 


- **N transistors**
- **No static consumption**

Example: AND Gate

 

NMOS-Only Logic

  


Tail end of transient very slow due to the small current available


Complementary Pass Transistor Logic




(a)

 

AND/NAND

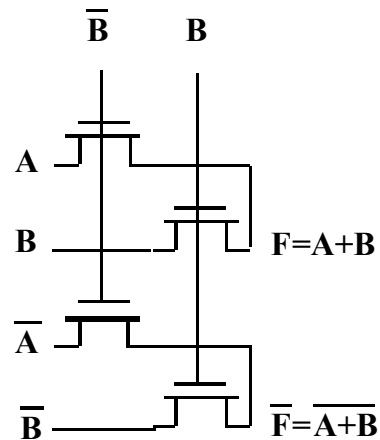

OR/NOR

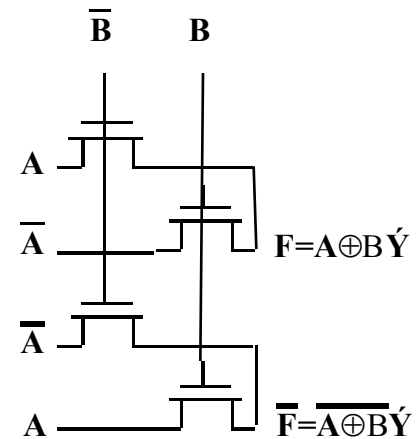




EXOR/NEXOR

(b)



Complementary Pass Transistor Logic

- Complementary data inputs and outputs are always available
- Output are always connected to low-impedance
- Design is very modular. The same topology is used. Permutation of inputs is used.
- Complementary signals have to be routed
- Restorer has to be used, otherwise static consumption


Solution: Transmission Gate

   



Pass-Transistor Based Multiplexer

  

Transmission Gate XOR

 


Resistance of Transmission Gate

  


It has a series resistance that can be assumed constant, and equal to a couple of $k\Omega$


Delay in Transmission Gate Networks

 

(a)

 

(b)

 

(c)

Delay Optimization

- **Delay of RC chain**

$$t_p = 0.69 \sum_{k=0}^n CR_{eq}^k = 0.69 CR_{eq} \frac{n(n+1)}{2}$$

- **Delay of Buffered Chain**

$$\begin{aligned} t_p &= 0.69 \left[\frac{n}{m} CR_{eq} \frac{m(m+1)}{2} \right] + \left(\frac{n}{m} - 1 \right) t_{buf} \\ &= 0.69 \left[CR_{eq} \frac{n(m+1)}{2} \right] + \left(\frac{n}{m} - 1 \right) t_{buf} \end{aligned}$$

$$m_{opt} = 1.7 \sqrt{\frac{t_{pbuf}}{CR_{eq}}}$$



m_{opt} is typically 3 or 4 ..

Dynamic Logic

Dynamic CMOS

- In **static** circuits at every point in time (except when switching) the output is connected to either GND or V_{DD} via a low resistance path.
 - fan-in of n requires $2n$ (n N-type + n P-type) devices
- **Dynamic** circuits rely on the temporary storage of signal values on the capacitance of high impedance nodes.
 - requires on $n + 2$ ($n+1$ N-type + 1 P-type) transistors

Dynamic Gate

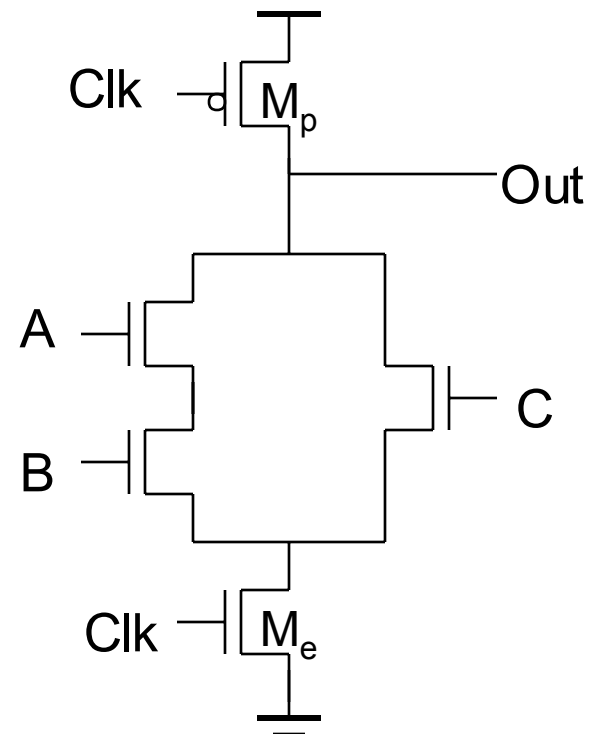 


Two phase operation

Precharge (CLK = 0)

Evaluate (CLK = 1)


Dynamic Gate

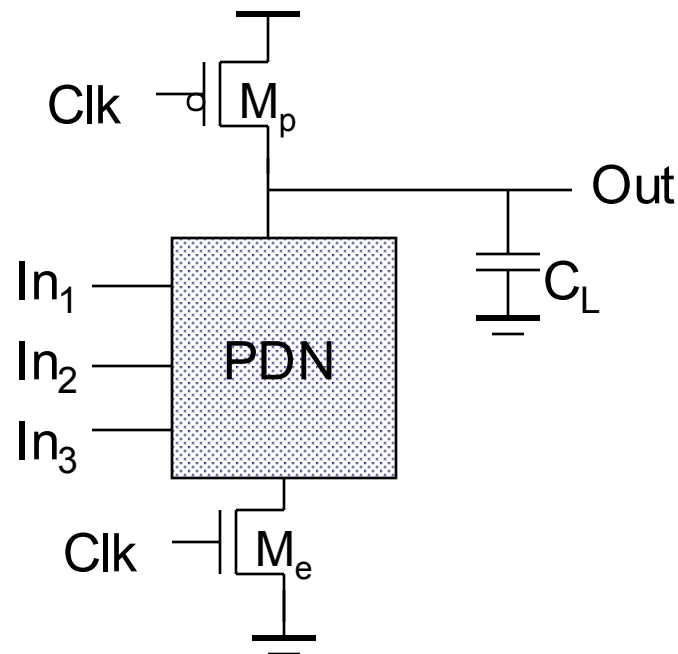

Two phase operation

Precharge (Clk = 0)

Evaluate (Clk = 1)

 

Conditions on Output

- Once the output of a dynamic gate is discharged, it cannot be charged again until the next precharge operation.
- Inputs to the gate can make **at most** one transition during evaluation.
- Output can be in the high impedance state during and after evaluation (PDN off), state is stored on C_L


Properties of Dynamic Gates

- Logic function is implemented by the PDN only
 - number of transistors is $N + 2$ (versus $2N$ for static complementary CMOS)
- Full swing outputs ($V_{OL} = GND$ and $V_{OH} = V_{DD}$)
- Non-ratioed - sizing of the devices does not affect the logic levels
- Faster switching speeds
 - reduced load capacitance due to lower input capacitance (C_{in})
 - reduced load capacitance due to smaller output loading (C_{out})
 - no I_{sc} , so all the current provided by PDN goes into discharging C_L


Properties of Dynamic Gates

- Overall power dissipation usually higher than static CMOS
 - no static current path ever exists between VDD and GND (including Psc)
 - no glitching
 - higher transition probabilities due to periodic charge and discharge
 - extra load on Clk
- PDN starts to work as soon as the input signals exceed V_{Tn} , so V_M , V_{IH} and V_{IL} equal to V_{Tn}
 - low noise margin (NML)
- Needs a precharge/evaluate clock

Issues in Dynamic Design: Charge Leakage

 


Leakage sources

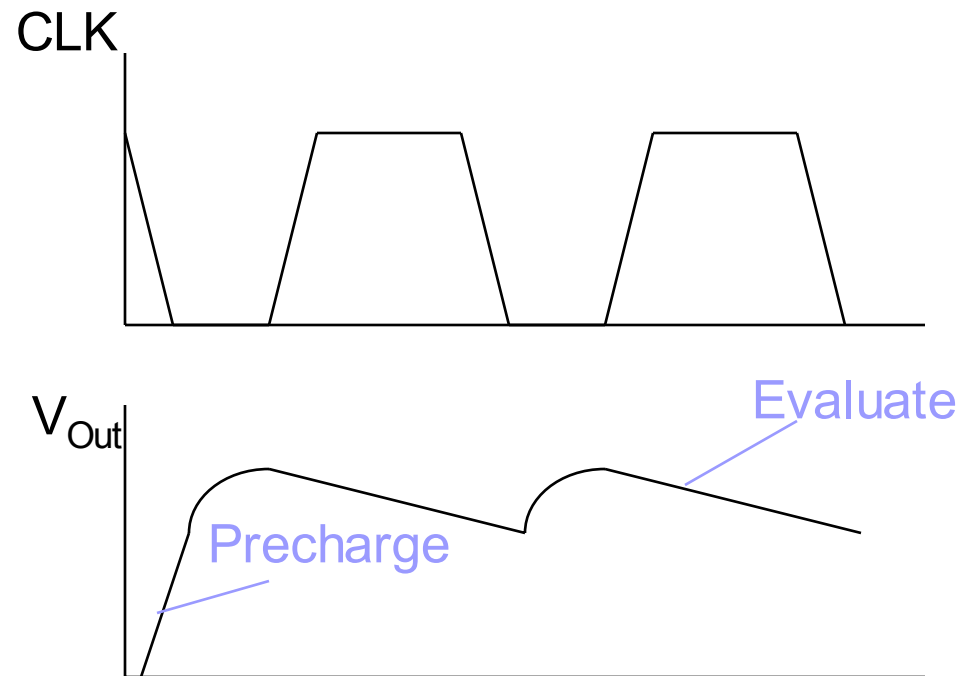


Dominant component is subthreshold current

Issues in Dynamic Design: Charge Sharing

 

Charge stored originally on C_L is redistributed (shared) over C_L and C_A leading to reduced robustness

 
Issues in Dynamic Design: Backgate Coupling



Dynamic NAND

Static NAND

 Issues in Dynamic Design 4: Clock Feedthrough



Coupling between Out and Clk input of the precharge device due to the gate to drain capacitance. So voltage of Out can rise above V_{DD} . The fast rising (and falling edges) of the clock **couple** to Out.