 




Introducción a VLSI

EAMTA 2006






Introducción a VLSI

Clase 4: Lógica Secuencial y Subsistemas

Programa

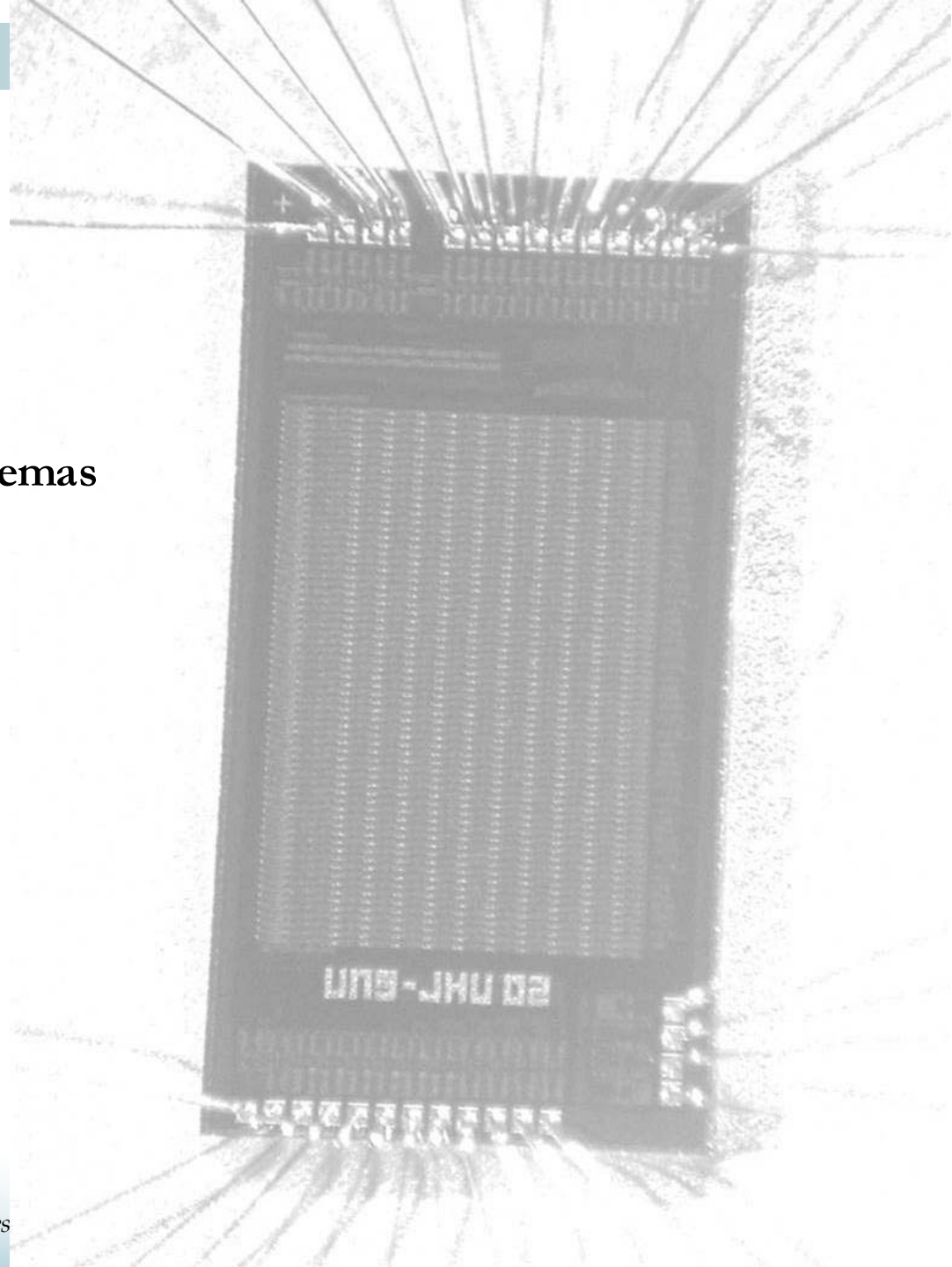- El Transistor MOS
- Layers y Layout
- Lógica Combinacional
- **Lógica Secuencial y Subsistemas**




Organización

- Lógica secuencial
- Sumadores
- Otros subsistemas
- Memorias

Sequential Logic Circuits

Sequential Logic

 


2 storage mechanisms

- positive feedback
- charge-based


Naming Conventions

- In our text:
 - a latch is level sensitive
 - a register is edge-triggered
- There are many different naming conventions
 - For instance, many books call edge-triggered elements flip-flops
 - This leads to confusion however


Timing Definitions

 

Characterizing Timing

 


Register

 

Latch

Maximum Clock Frequency

 

$$t_{clk-Q} + t_{p,comb} + t_{setup} = T$$

Also:

$$t_{cdreg} + t_{cdlogic} > t_{hold}$$



t_{cd} : contamination delay =
minimum delay

Data is hold long enough
so it can be output

Latch versus Register



□ Latch

stores data when
clock is low

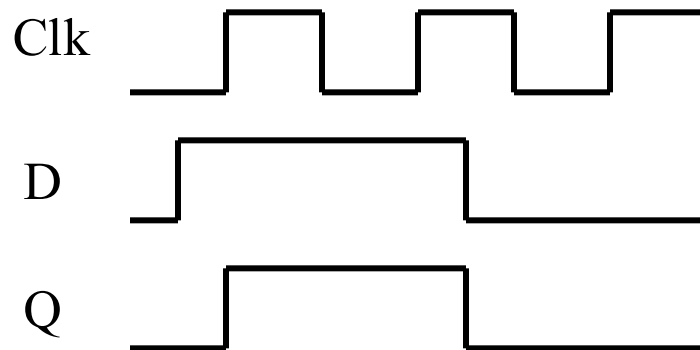 


■ Register

stores data when
clock rises

  


Latches

Positive Latch

 


Negative Latch

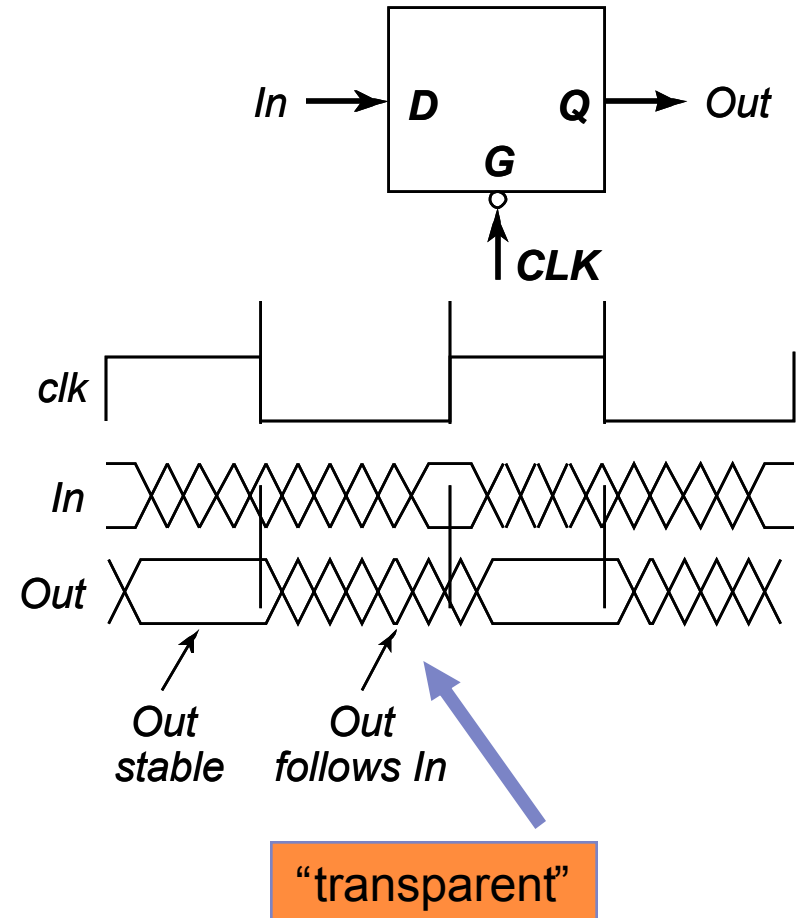


Storage Mechanisms

Static

 


Dynamic (charge-based)

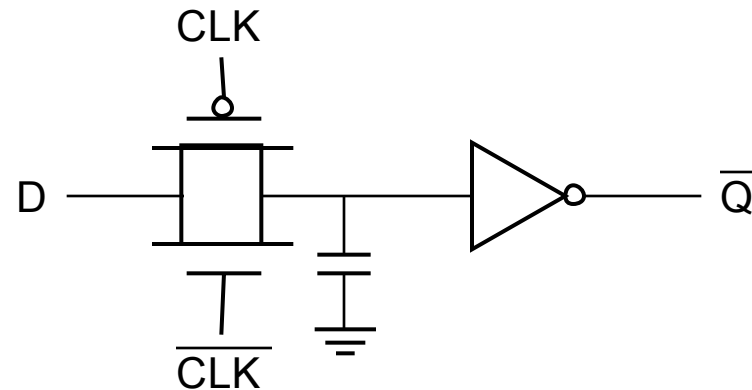

Race might occur with a master-slave


Mux-Based Latches

Negative latch
(transparent when CLK= 0)

 


$$Q = \overline{Clk} \cdot Q + Clk \cdot In$$

Positive latch
(transparent when CLK= 1)

 


$$Q = Clk \cdot Q + \overline{Clk} \cdot In$$

Mux-Based Latch

 


Number of transistor that the clock has to drive is an important metric.
In this case, there are 4 (four) transistors in the CLK line


Mux-based latch

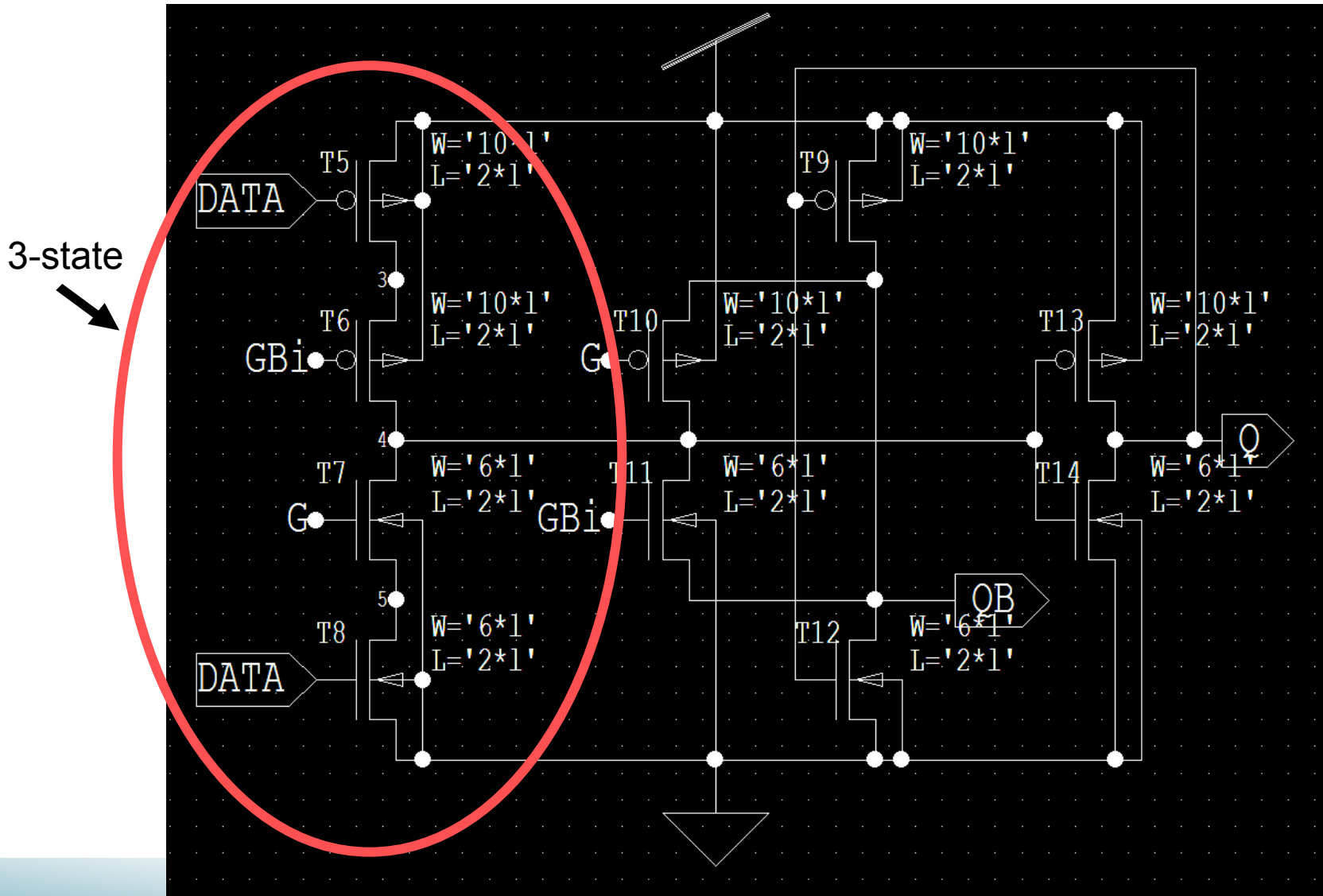


Mux-based latch

 

Mux-Based Latch

 

NMOS only

 


Non-overlapping clocks


Simple but degrades a High input to $V_{dd} - V_{tn}$

Master-Slave Register


Multiplexer-based latch pair

 


DFF PC

 


DFF PC

 

Avoiding Clock Overlap

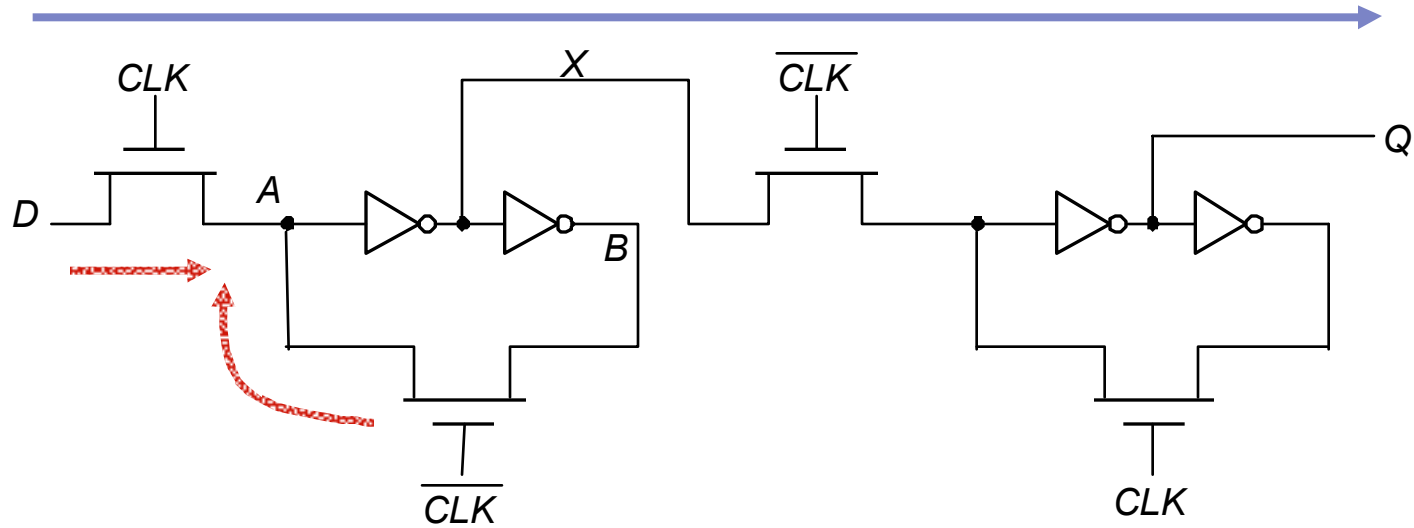

(a) Schematic diagram

 


(b) Overlapping clock pairs

CLK and $CLKB$ are 1 at the same time, then D passes directly to output (race)

Output can change in the rising edge of the CLK for a negative edge-triggered FF


Non-overlapping Clocks

 

 (a) Schematic diagram

CLK1 and CLK2 are non-overlapping



T non-overlap has to be small enough so that the charge in the intermediate nodes is preserved (gates are in tri-state)



(b) Non-Overlapping clock pairs

Overpowering the Feedback Loop — Cross-Coupled Pairs



NOR-based set-reset

  

S	R	Q	$\bar{Q}$
0	0	Q	$\bar{Q}$
1	0	1	0
0	1	0	1
1	1	0	0

Forbidden State


Clocked SR

 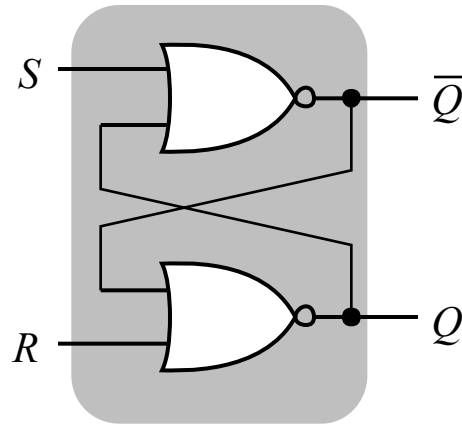


This is not used in datapaths any more, but is a basic building memory cell

Transistors M5-M6 (M7-M8) has to be sized to overpower M2 (M4) and pull that node down

Sizing Issues

 


 Output voltage dependence
on transistor width



Transient response


Other Latches/Registers: C²MOS

 


“Keepers” can be added to make circuit pseudo-static

Insensitive to Clock-Overlap

Hold time must be imposed

 

(a) (0-0) overlap

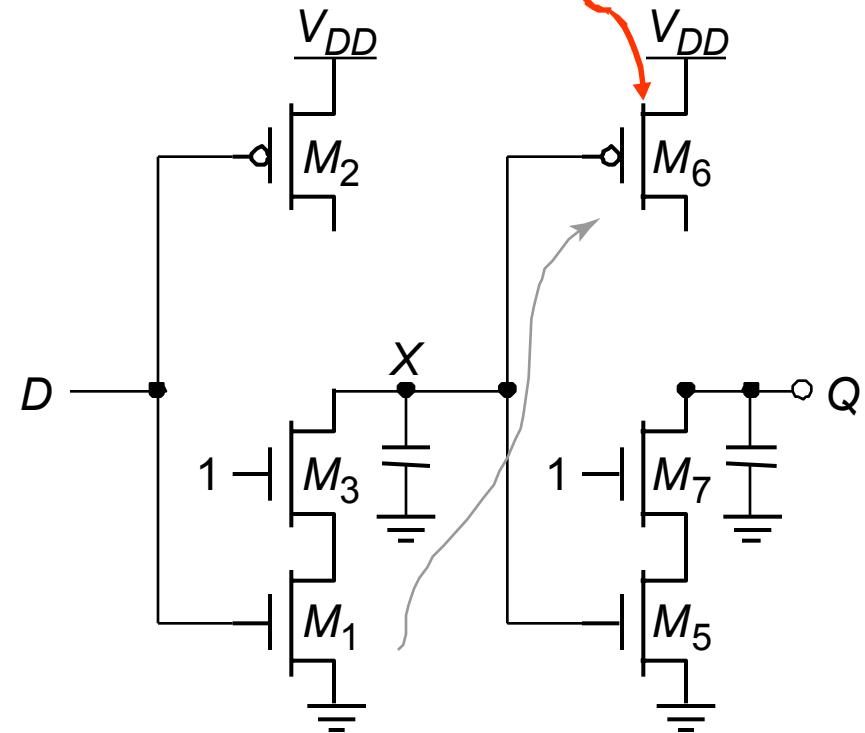

(b) (1-1) overlap

Insensitive as long as the rise and fall times are sufficiently small

Adders

Adders

- Important subsystem in digital design, so we care about performance
- Good example of ways to think about building systems larger than 1-2 gates
- Basic problem: Bit N of the result depends on $0 - (N-1)$ input bits.
 - Could build separate circuits to compute partial sums
 - Fast but very Big
 - Use bit adders that compute the value of each bit and connect them together to form N -bit adders

Half adders

For a one-bit add, the sum is just the XOR of the inputs, and the carry out is just the AND

$$S = A \oplus B$$

A	B	Sum	Carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

Cells that compute this function are called *half-adders*

Full adders

To get a cell that we can compose into a multi-bit adder, we need to have a carry in input as well.

- These are called full adders

C_{in}	A	B	$AB(G)$	$A+B(P)$	$A \oplus B(P)$	S	C_{out}
0	0	0	0	0	0	0	0
0	0	1	0	1	1	1	0
0	1	0	0	1	1	1	0
0	1	1	1	1	0	0	1
1	0	0	0	0	0	1	0
1	0	1	0	1	1	0	1
1	1	0	0	1	1	0	1
1	1	1	1	1	0	1	1


$$S = ABC_{in} + (A + B + C_{in})\overline{C_{out}}$$

$$C_{out} = AB + (A + B)C_{in}$$

Note that the carry-out can be *generated* when A and B are true, or *propagated* if A or B are true and C_{in} is true

Multi-Bit adders


 
- By simply cascading full-adder blocks, we obtain an n-bit adder:



- The time required to complete an addition is limited by the carry bit *rippling* through the structure.
- Worst case, a carry will ripple all the way through from least significant bit to most significant bit.


Gate level implementation

  Much more worried about the delay from $A, B, C_{in} \rightarrow C_{out}$ than $A, B, C_{in} \rightarrow \text{Sum}$




Better full adder (Mirror adder)

 - We can improve the delay by using the following implementation:




- Notice that the n- and p-networks are not duals!

Bit slice layout

 


Bit slice layout

 


Multi-bit adders can be obtained by repeating automatically the cell

Bit-slice Full Adder

 


Eight-bit Adder

 


Serial Adder

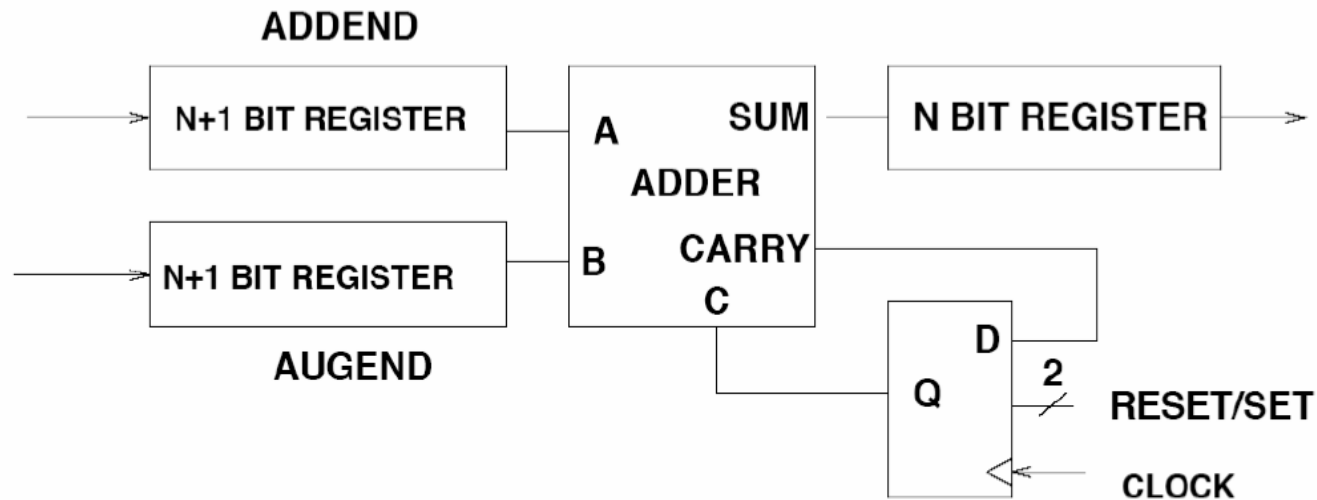- Ripple-carry adder has latency proportional to number of bits -- why not just re-use the same full adder for each bit?
 - In this case, want to equalize delay of sum and carry bits



Datapath organization

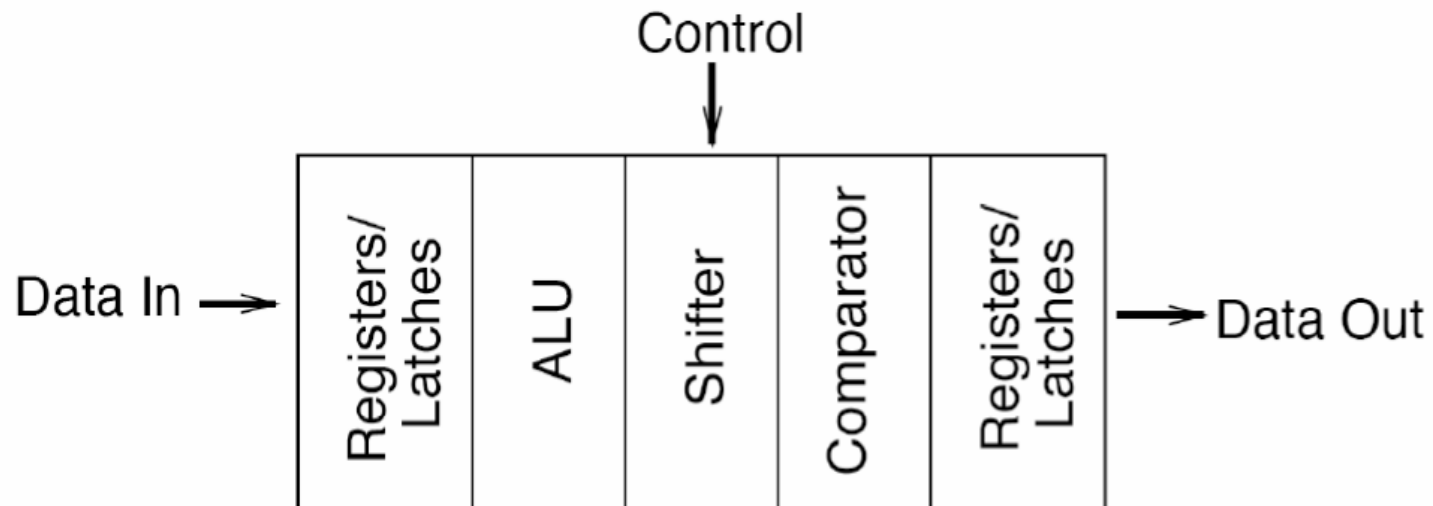- Microprocessors (and many other systems) are made up of a regular datapath and irregular control logic.
- In a microprocessor, the datapath is a functional block so flexible that it becomes programmable




Datapath organization

Drive data horizontally through the datapath

Control signals arrive vertically

Allows designer to stack different function units together

 Power, ground, clock typically run parallel to control



Subtraction

Exploit 2's complement notation

- $-X$ is generated by inverting each bit in X and adding one to the result
- Used because $X + -X = 0$ with this representation for $-X$


Subtractor is then adder with one input inverted and carry in = 1

- Can build adder/subtractor by XORing each bit of one input with subtract signal and using subtract as carry in

Otros Subsistemas

Comparison

 
- Want to compare two numbers, A and B
- If $A=B$, $A-B=0$
- If $B \geq A$, $A-B$ will generate a carry out in the last bit (overflow)
- Comparison can be implemented using a subtractor



Parity


- A binary word is said to have even (odd) *parity* if it has an even (odd) number of 1 bits.
- A parity generator indicates the parity of a binary word.
- Functionally, parity generation is as simple as an exclusive-OR:
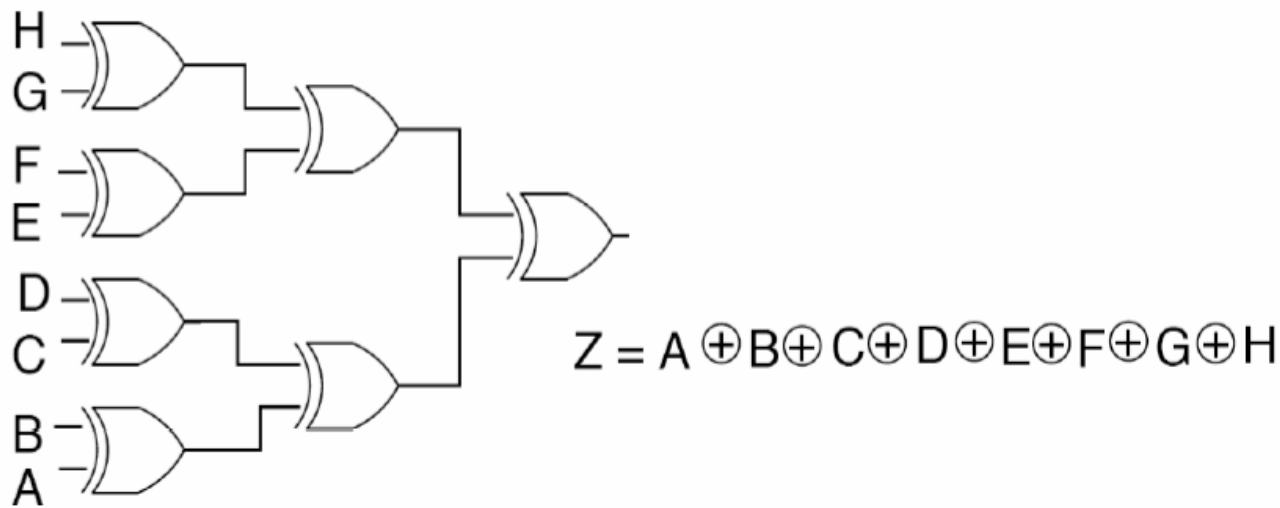
$$P_X = x_{n-1} \oplus x_{n-2} \oplus \cdots \oplus x_1 \oplus x_0$$



Crossbar as shifter

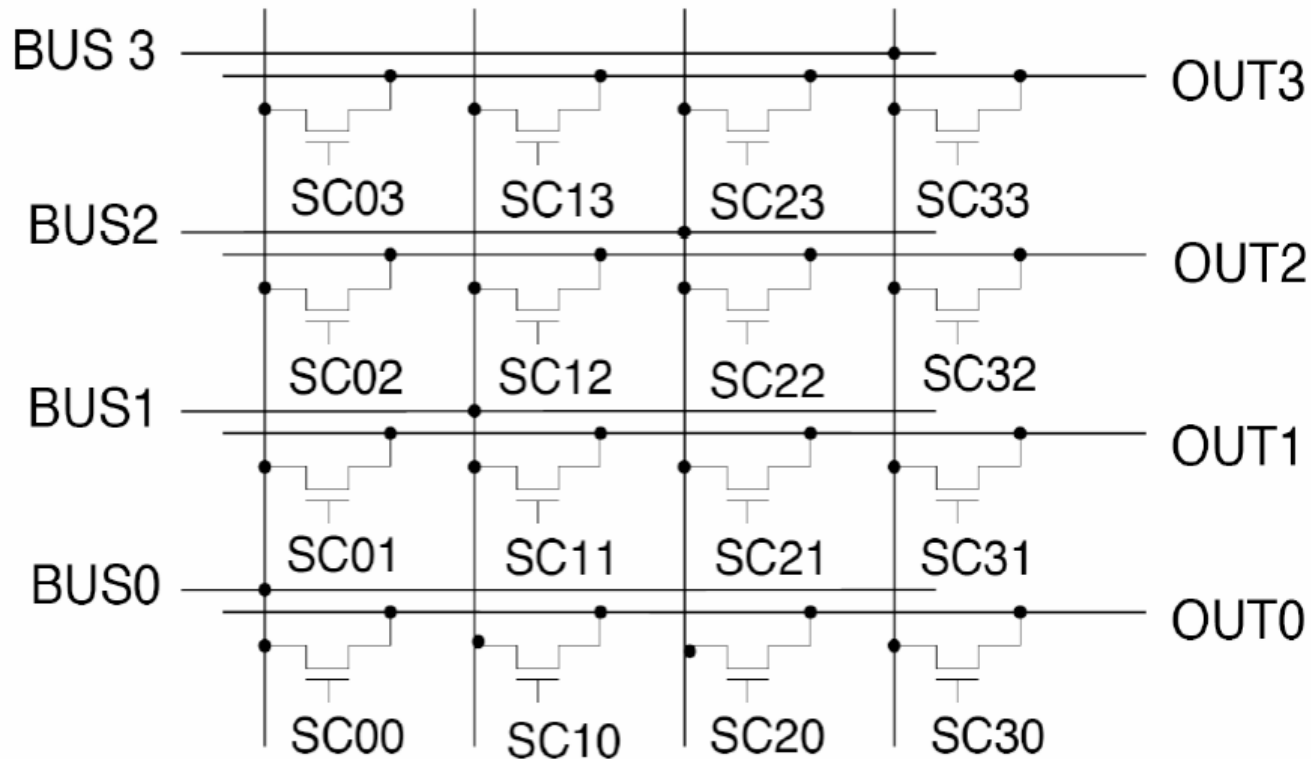- Can use a crossbar network to implement a shifter (and any other permutation of input bits)
 - Requires n^2 control inputs for n -bit data



Counters

Counts the number of events on its input



RULE # 1 of making a digital system work right: never gate clock signal !!

This is an asynchronous counter

- Bits don't switch in synchrony
- Count ripples through the bits

Counter

  - Adder with a constant input
- Selection used to define up (sum) or down (subtraction)
- Synchronous – all signals change with clock



Multiplication

- Single-bit multiplication is just AND

a	b	$a \times b$
0	0	0
0	1	0
1	0	0
1	1	1

- Multi-bit multiplication can be done by combination of AND, ADD, shift

Performance question #1: How many bit multiplications do you do at the same time?


- 1 (serial)
- Between 1 and n^2 (serial-parallel)
- All of them (parallel)

Trade-off between area and speed

Parallel Multiplication


Each *partial product* bit of the multiplication can be computed in parallel

 Then, perform n n -bit adds to sum the partial products




Serial-Parallel multiplier


- Requires $M+N$ clock cycles

 

Pipeline technique

 


Reference

 

Pipelined


Clock Period	Adder	Absolute Value	Logarithm
1	$a_1 + b_1$		
2	$a_2 + b_2$	$ a_1 + b_1 $	
3	$a_3 + b_3$	$ a_2 + b_2 $	$\log(a_1 + b_1)$
4	$a_4 + b_4$	$ a_3 + b_3 $	$\log(a_2 + b_2)$
5	$a_5 + b_5$	$ a_4 + b_4 $	$\log(a_3 + b_3)$

Pipelined Serial to Parallel

 

Memories


Organization

 

ROM

Simplest ROM cell is a single transistor


 
Precharge all bit lines high, assert word line. Transistors pull bits whose output = 0 low.





SRAM

Cross-coupled inverters hold state

  To write, drive data strongly on bit lines, such that you overwhelm the stored value




Static row decoder

 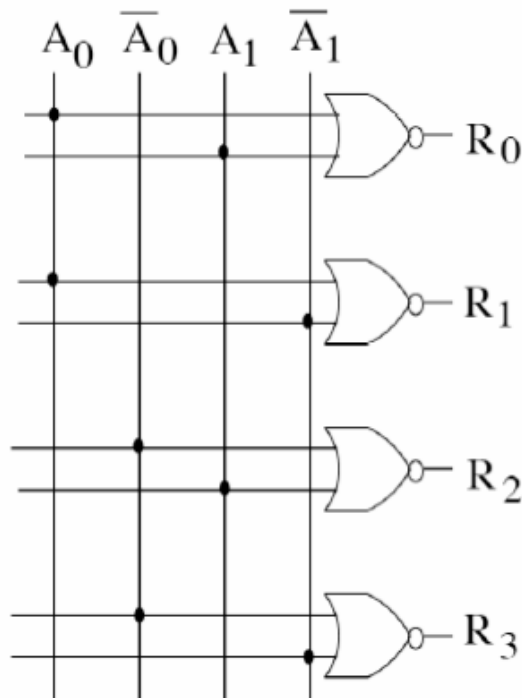

Due to the high capacitance of the word lines and the high number of address lines, these circuits have to be designed very carefully.

Row decoder

 simple tree decoder selects one out of 8 bits:



An alternative design is to use a structure similar to the row decoder to generate a one-hot drive signal based on the address bits

- Put full pass-gate at the output of each bit line, control signal to pass-gates are the outputs of the decoder
- Gives full output swings
- Fewer transistors in series --> faster
- May take more area, especially when you consider the number of control wires