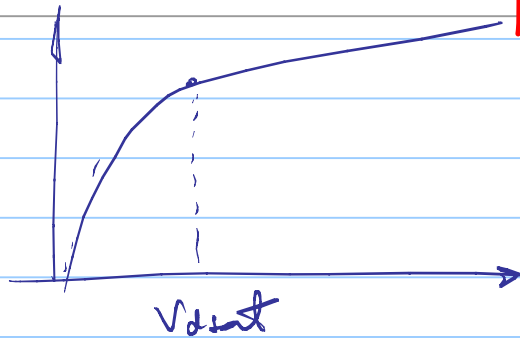


# CALCULO DE Req.

Note Title

12/5/2006



Modelo: 1)  $I_D = I_{D_{SAT}}$ .

2)  $I_D = I_{D_{SAT}} \cdot (1 + \lambda V_{DS})$ .

El cálculo de Req de acuerdo a  $t_p$ .

a) La descarga del cap.  $C_L$  es

$$I_{D_{SAT}} = C_L \cdot \frac{V_{DD}}{2 \cdot t_p} \quad t_p = \frac{V_{DD} \cdot C_L}{2 I_{D_{SAT}}}$$

La descarga en un circuito RC es

$$V(t) = V(t_0) \cdot e^{-t/RC}$$

$$\text{Si } V(t) = V(t_0)/2 \rightarrow \frac{1}{2} = e^{-t/RC}$$

$$e^{-t/RC} = \frac{1}{2} \quad \frac{t_p}{RC} = \ln(2) \quad t_p = \ln(2) RC$$

$$\text{Luego } \frac{V_{DD}}{2 I_{D_{SAT}}} = \ln(2) Req$$

$$Req = \frac{1}{2 \ln(2)} \cdot \frac{V_{DD}}{I_{D_{SAT}}}$$

Suponhamos ainda  $I_D = I_{D_{SAT}} \cdot (1 + \lambda \cdot (V_{DS} - V_{D_{SAT}}))$

$$I_D = C_L \frac{dV_0}{dt} \rightarrow dt = \frac{C_L}{I_{D_{SAT}} (1 + \lambda \cdot (V_{DS} - V_{D_{SAT}}))} dV_0$$

$$\int_{t_i}^{t_f} dt = t_p = \frac{C_L}{I_{D_{SAT}}} \int_{V_{DD}/2}^{V_{DD}} \frac{1}{1 + \lambda \cdot (V_0 - V_{D_{SAT}})} dV_0$$

$$t_p = \frac{C_L}{I_{D_{SAT}}} \cdot \frac{\log(1 + \lambda \cdot (V_0 - V_{D_{SAT}}))}{\lambda} \Bigg|_{V_{DD}/2}^{V_{DD}}$$

$$t_p = \frac{C_L}{I_{D_{SAT}} \lambda} \cdot \log \frac{1 + \lambda \cdot (V_{DD} - V_{D_{SAT}})}{1 + \lambda \cdot (\frac{V_{DD}}{2} - V_{D_{SAT}})}$$

$$= \frac{C_L}{\lambda I_{D_{SAT}}} \cdot \log \frac{I_{D_{SAT}} (1 + \lambda (V_{DD} - V_{D_{SAT}}))}{I_{D_{SAT}} (1 + \lambda (\frac{V_{DD}}{2} - V_{D_{SAT}}))}$$

$$= \frac{C_L}{\lambda I_{D_{SAT}}} \cdot \log \frac{I_D(V_{DD})}{I_D(V_{DD}/2)}$$

Calculo de  $\lambda$ .  $\lambda = \frac{I_D(V_{DD}) - I_D(V_{DD}/2)}{I_{D_{SAT}} \cdot \frac{1}{V_{DD}/2}}$

$$t_p = \frac{C_L \cdot (V_{DD}/2)}{I_D(V_{DD}) - I_D(V_{DD}/2)} \cdot \log \frac{I_D(V_{DD})}{I_D(V_{DD}/2)}$$

$$t_p = \frac{1}{2} \frac{C_L V_{DD}}{(I_D^2 - I_D^1)} \cdot \log \frac{I_D^2}{I_D^1}$$

$$Req = \frac{1}{2 \times \ln(2)} \cdot \frac{V_{DD}}{I_D^2 - I_D^1} \cdot \log \frac{I_D^2}{I_D^1}$$

En forma analítica

$$t_p = \frac{C_L}{\lambda \cdot K \cdot S \cdot \left( V_{DD} - V_T - \frac{V_{DSAT}}{2} \right) V_{DSAT}} \log \frac{I_D(V_{DD})}{I_{D0}(V_{DD0})}$$

o

$$t_p = \frac{C_L}{\lambda \cdot K \cdot S \cdot \left( V_{DD} - V_T - \frac{V_{DSAT}}{2} \right) V_{DSAT}} \times \log \frac{1 + \lambda(V_{DD} - V_{DSAT})}{1 + \lambda\left(\frac{V_{DD}}{2} - V_{DSAT}\right)}$$

Ejemplo:  $MM5 \ 0,5 \mu$ .  $\frac{W}{L} = \frac{1,8 \mu}{0,6 \mu}$ .  $C_L = 100 \text{ fF}$

SPICE:  $I_D(V_{DD}) = 568 \mu\text{A}$

$$I_D\left(\frac{V_{DD}}{2}\right) = 535 \mu\text{A}$$

$$t_{p(H-L)} = 483 \text{ ps.}$$

Cálculo  $t_p = 453 \text{ ps.}$

Nota: 23 ps son de error debido al ruido de la simulación.  $t_{p(H-L)}(\text{correg}) = 460 \text{ ps.}$

$$\text{Si tomamos } I_{D_{SAT}}' = \frac{I_{D_{SAT}}}{2} \left( (1 + \lambda V_{DD}) + \frac{(1 + \lambda V_{DD})}{2} \right)$$

$$= I_{D_{SAT}} \left( \frac{1}{2} + \frac{1}{2} \lambda V_{DD} + \frac{1}{2} + \frac{1}{4} \lambda V_{DD} \right) =$$

$$= I_{D_{SAT}} \left( 1 + \lambda \cdot V_{DD} \left( \frac{1}{2 \cdot 2} + \frac{1}{4} \right) \right) =$$

$$= I_{D_{SAT}} \cdot \left( 1 + \frac{3}{4} \lambda \cdot V_{DD} \right).$$

$$y \quad R_{eq} = \frac{1}{2 \ln(2)} \frac{V_{DD}}{I_{D_{SAT}} \cdot \left( 1 + \frac{3}{4} \lambda V_{DD} \right)}$$

Tomemos la expresión de  $I_{D_{SAT}}$

$$I_{D_{SAT}} = \mu C_{ox} \frac{W}{L} \cdot V_{D_{SAT}} \left( V_{GS} - V_T - \frac{V_{D_{SAT}}}{2} \right)$$

y evaluemos para  $V_{GS} = V_{DD}$ .

$$I_{D_{SAT}} = 2 \cdot k_N \cdot V_{D_{SAT}} \left( V_{DD} - V_T - \frac{V_{D_{SAT}}}{2} \right)$$


$$y \quad R_{eq} = \frac{1}{2 \ln(2)} \frac{V_{DD}}{2 k_N V_{D_{SAT}} \left( V_{DD} - V_T - \frac{V_{D_{SAT}}}{2} \right) \cdot \left( 1 + \frac{3}{4} \lambda V_{DD} \right)}$$

Si es que se tiene en cuenta  $\lambda$ .

Caso contrario

$$R_{eq} = \frac{1}{2 \ln(2)} \cdot \frac{V_{DD}}{k'_N V_{DSAT} \left( V_{DD} - V_T - \frac{V_{DSAT}}{2} \right)} \quad (a)$$

Gráfica (a)

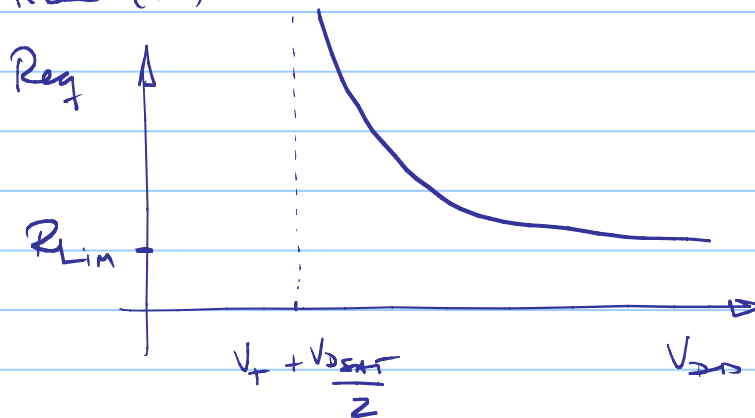

Valido solo para  
 $V_G > V_T + \frac{V_{DSAT}}{2}$

$$R_{Lim} = \frac{1}{2 \ln(2)} \cdot \frac{1}{k'_N V_{DSAT}}$$

Si utilizamos la expresión exacta


$$R_{eq} = \frac{1}{2 \ln(2)} \cdot \frac{V_{DD}}{2K_S \left( V_G - \frac{V_{DS}}{2} \right) V_{DS}} \cdot \frac{1}{\left( \frac{1 + V_{DS}}{E_C L} \right)}$$

$$\text{con } V_{DS} = \frac{E_C L \cdot V_G}{E_C L + V_G}$$

$$R_{eq} = \frac{1}{2 \ln(2)} \cdot \frac{V_{DD}}{2K_S \cdot \left( V_{DD} - V_T - \frac{E_C L \cdot (V_{DD} - V_T)}{2(E_C L + V_{DD} - V_T)} \right)} \cdot x$$

$$x = \frac{1}{\left( \frac{E_C L (V_{DD} - V_T)}{E_C L + V_{DD} - V_T} \right)} \cdot \frac{1}{\left( 1 + \frac{V_{DD} - V_T}{E_C L + V_{DD} - V_T} \right)}$$

La gráfica exacta:

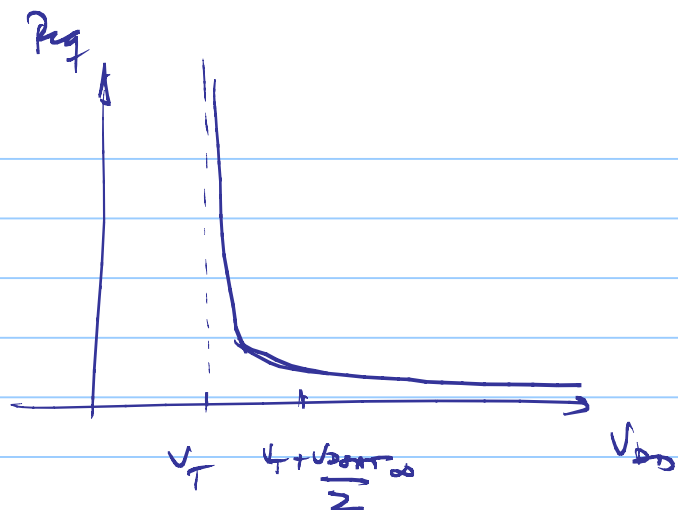

$$\text{En } V_{DS} = V_T + \frac{E_c L}{2}; \quad V_G' = V_{DD} - V_T = \frac{E_c L}{2}$$

$$V_{DS} = \frac{E_c L \cdot V_G'}{E_c L + V_G'} = \frac{E_c L \cdot \frac{E_c L}{2}}{\left(\frac{2E_c L}{2} + \frac{E_c L}{2}\right)} \cdot \frac{1}{2} = \frac{2}{3} \cdot \frac{1}{2} \cdot E_c L$$

$$\boxed{V_{DSAT} = \frac{E_c L}{3}}$$

$$R_{eq} = \frac{1}{2 \ln(2)} \cdot \frac{V_{DD}}{2kS \left( V_{DD} - \frac{E_c L}{2 \cdot 3} \right) \frac{E_c L}{3} \cdot \left( 1 + \frac{E_c L}{3 \cdot E_c L} \right)}$$

$$= \frac{1}{2 \ln(2)} \cdot \frac{V_{DD}}{2kS \left( V_{DD} - \frac{E_c L}{6} \right) \cdot \frac{E_c L}{3} \cdot \frac{4}{3}}$$

$$V_{DD} = V_T + \frac{E_c L}{2}; \quad R_{eq} = \frac{1}{2 \ln(2)} \cdot \frac{V_T + \frac{E_c L}{2}}{2kS \left( V_T - \frac{1}{3} E_c L \right) \cdot \frac{4}{9} E_c L} \rightarrow \infty$$